



ATHENS UNIVERSITY  
OF ECONOMICS  
AND BUSINESS


## Αρχιτεκτονική Υπολογιστών

ΠΡΩΤΗ ΕΡΓΑΣΙΑ


Στεφάνου Δημήτριος 3160245  
Σωτηροπούλου Δικαία 3160172  
Ομάδα 15

## RTLs

### AND Gate

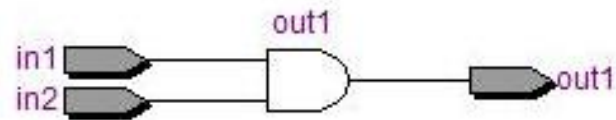


### AND Gate (16 bits)

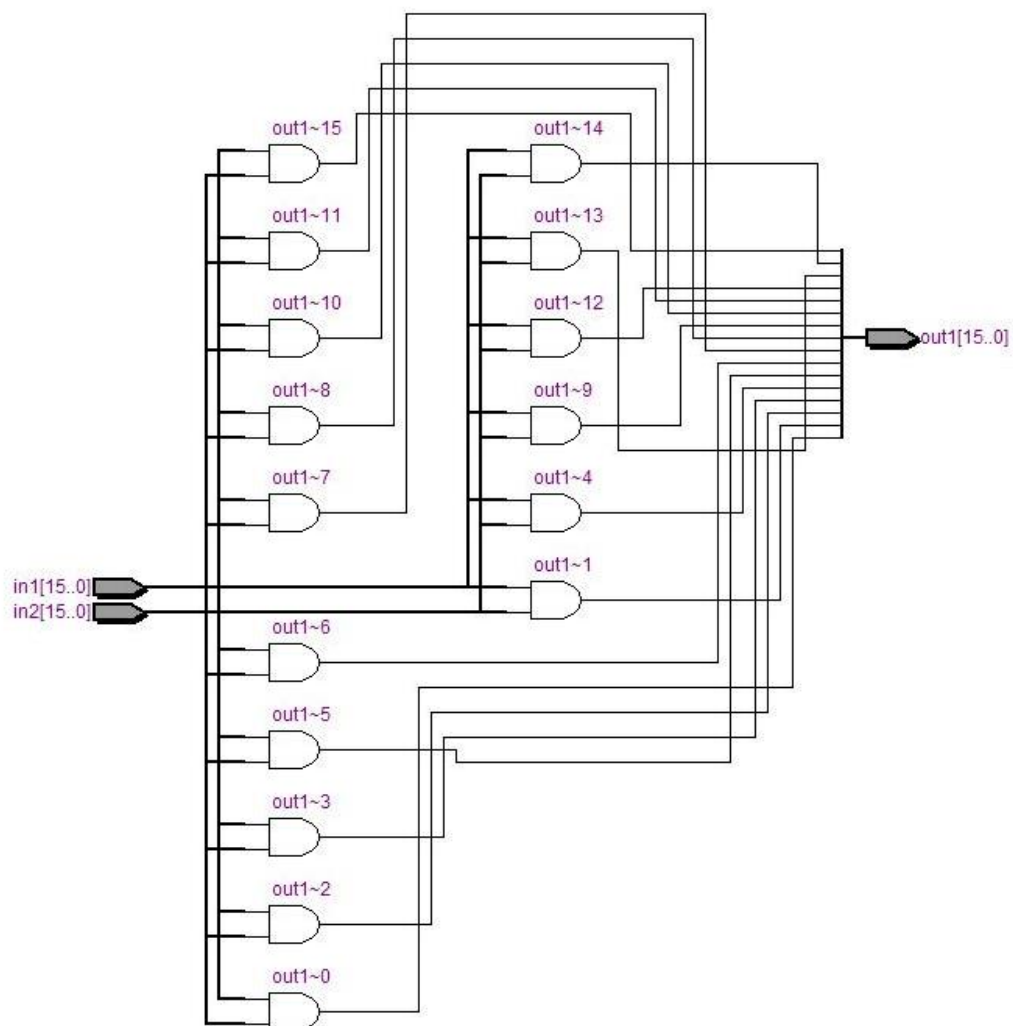


NOT Gate (16bits)




OR Gate (3 inputs)

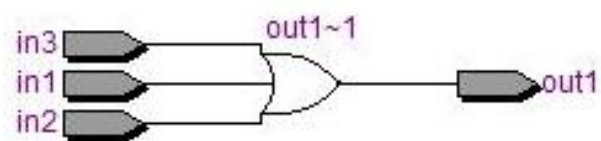


OR Gate (16 bits)

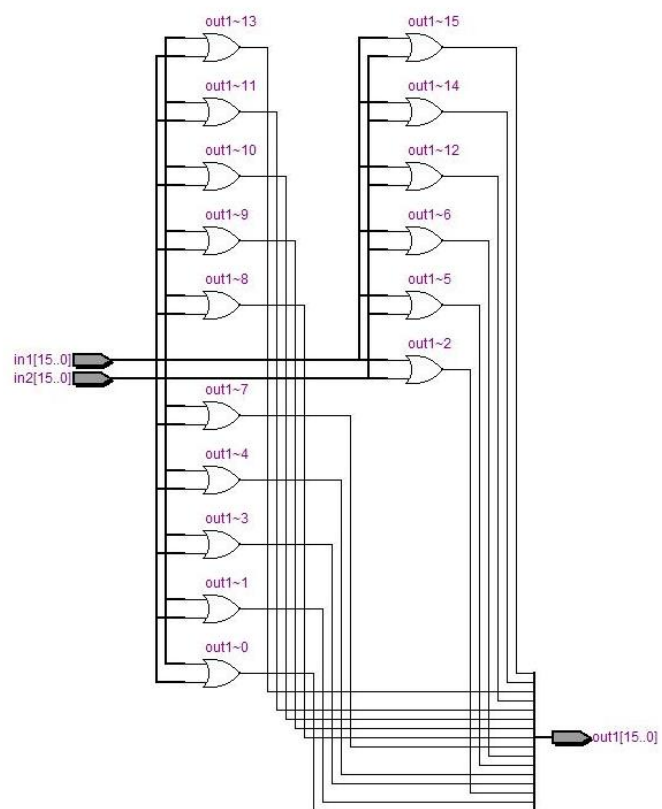


### XOR Gate

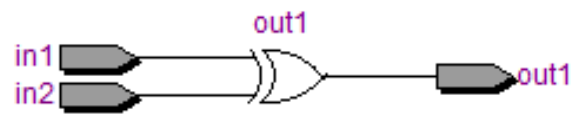

### XOR Gate (3 inputs)

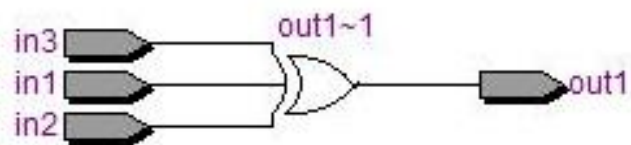


### NOT (ALU implementation)

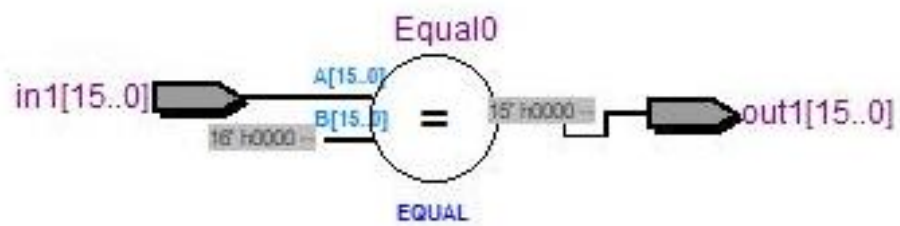



## Full Adder (1 bit)

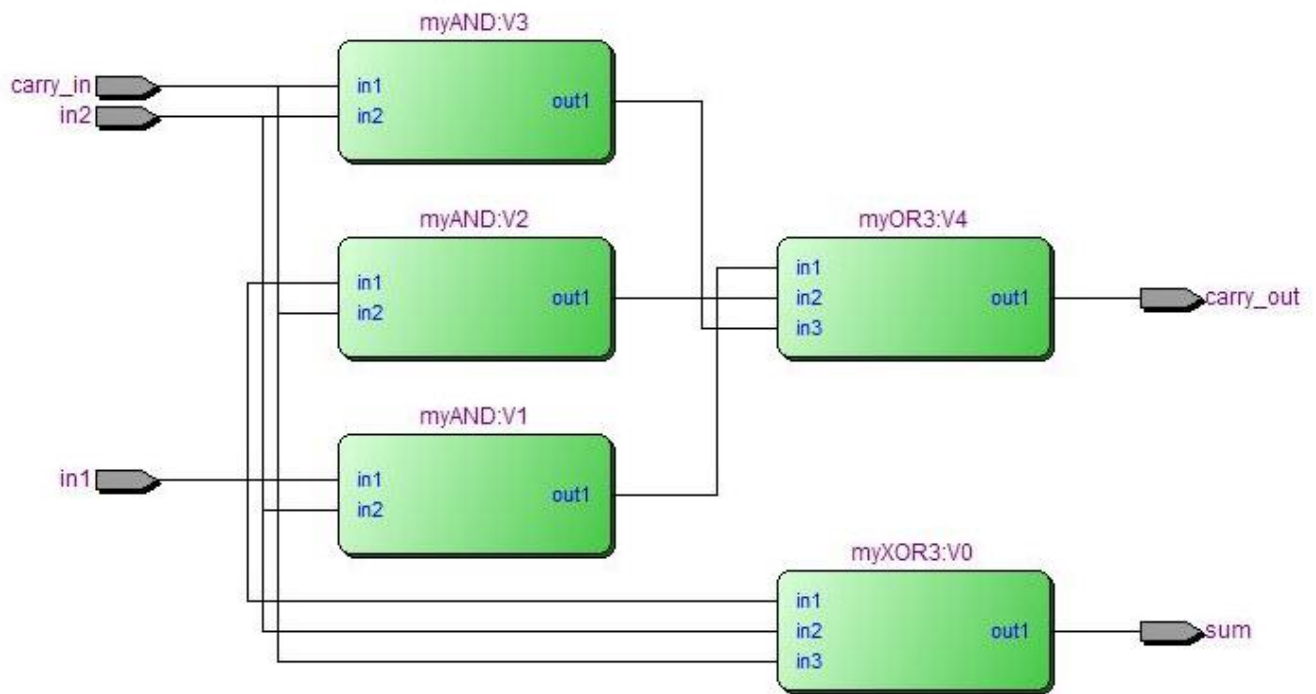


## Full Adder (16 bits)



## Multiplexer 2 to 1 (16 bits)




## Multiplexer 8 to 1

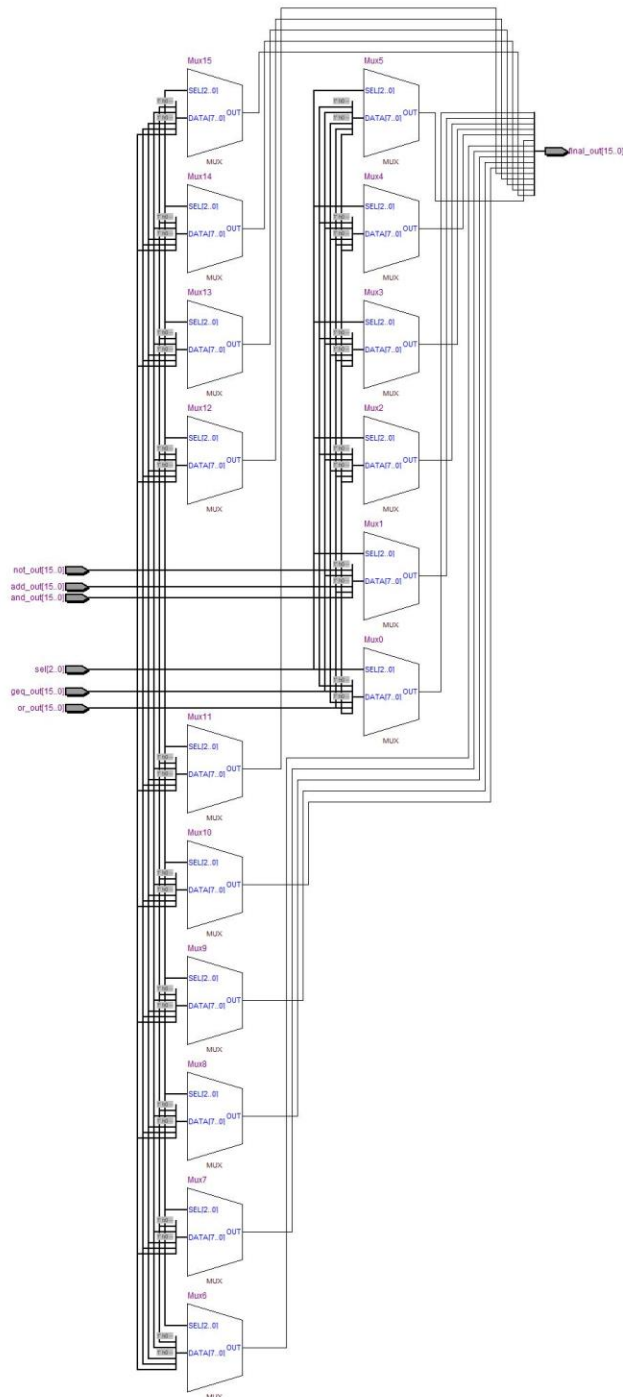




## ALU (16 bits)

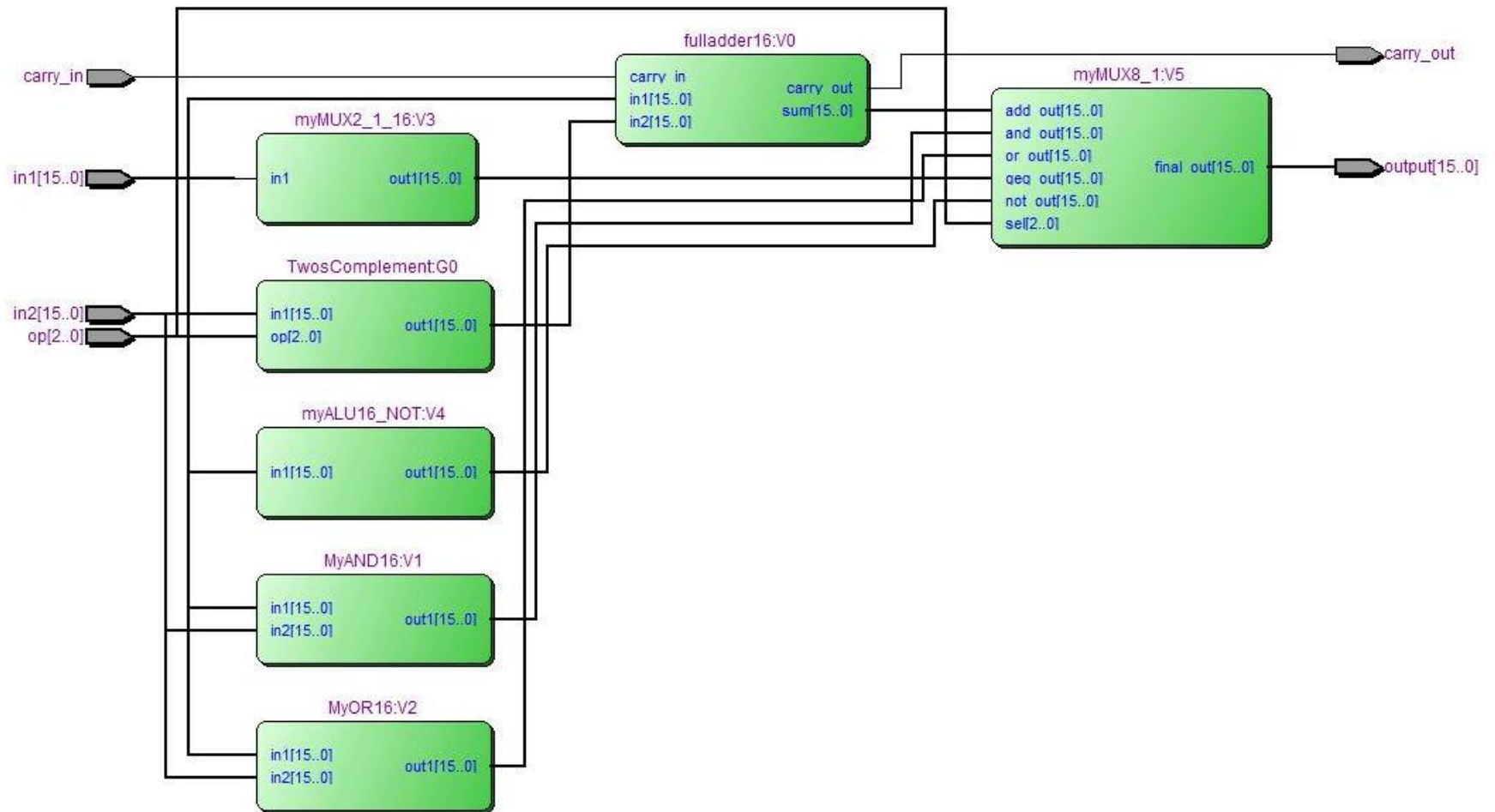


# Waveforms


## AND Waveform

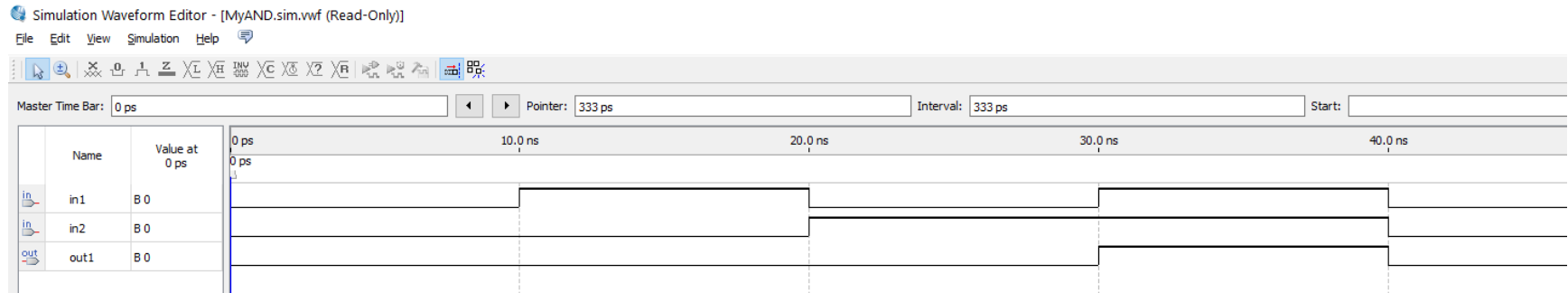


## AND (16 bit) Waveform

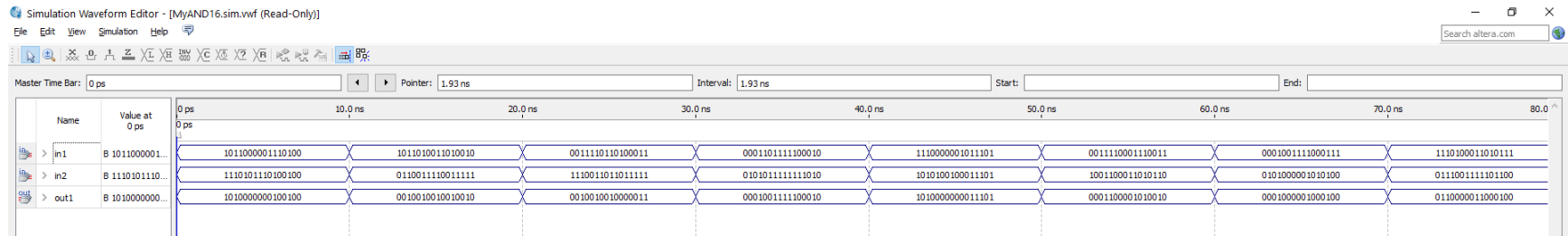


## NOT (16 bit) Waveform

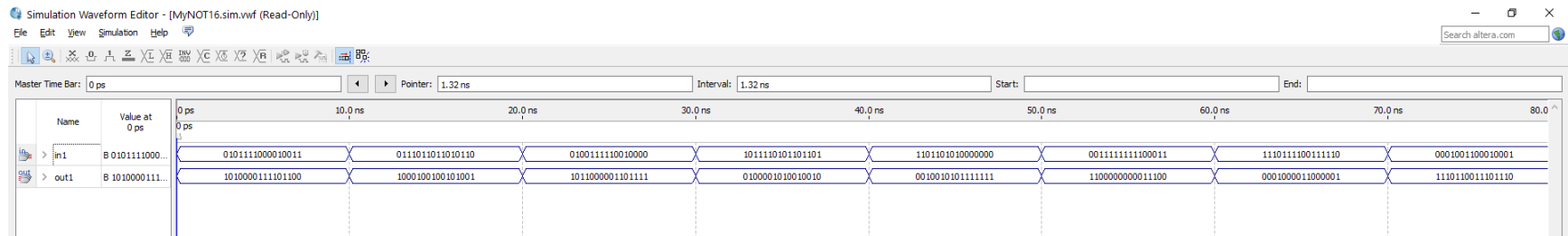


OR (3 inputs) Waveform

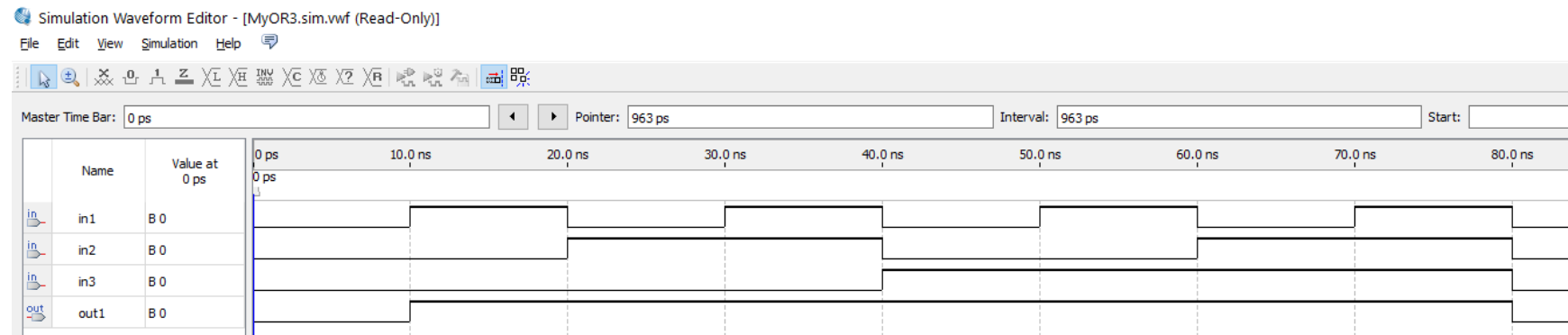

OR (16 bits) Waveform

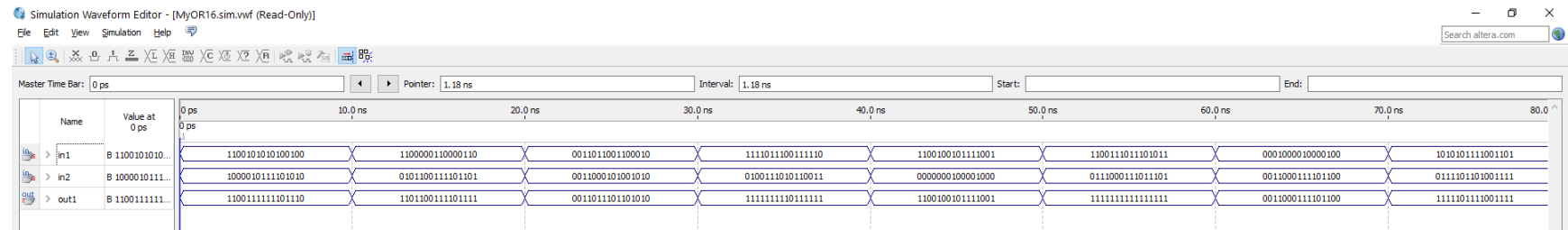


### XOR Waveform

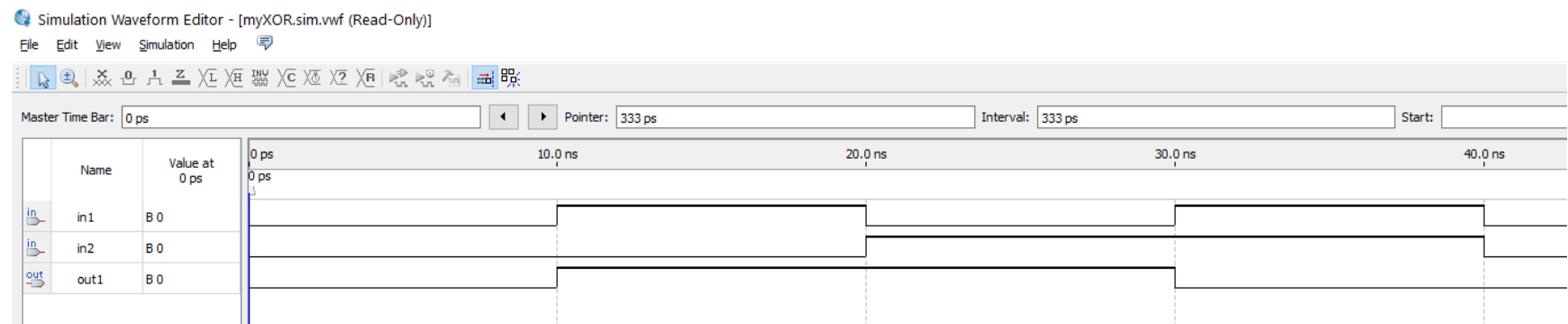

## XOR (3 inputs) Waveform

Simulation Waveform Editor - [MyXOR3.sim.vwf (Read-Only)]


File Edit View Simulation Help

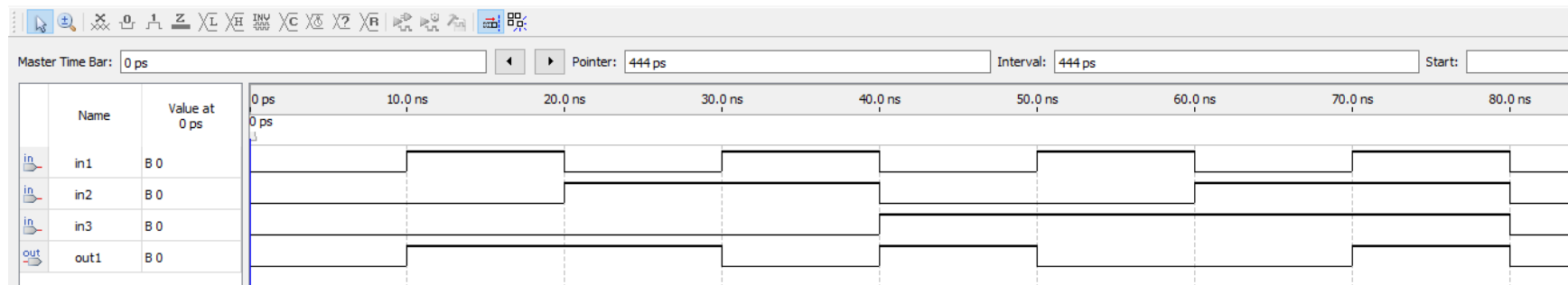

## NOT (ALU implementation) Waveform

Simulation Waveform Editor - [MyALU16\_NOT.sim.vwf (Read-Only)]


File Edit View Simulation Help

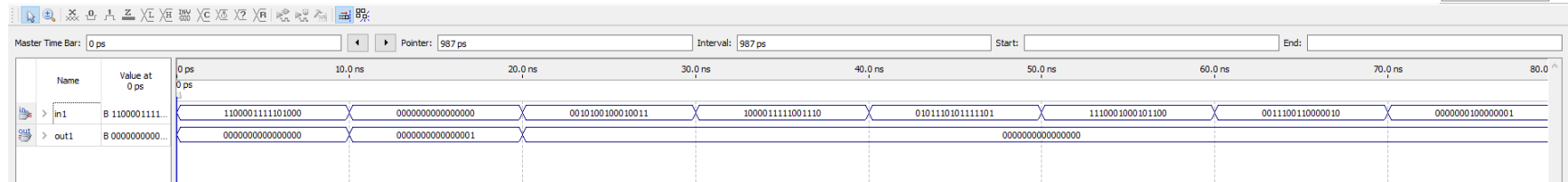

## Two's Complement

Simulation Waveform Editor - [TwosComplement.sim.vwf (Read-Only)]


File Edit View Simulation Help

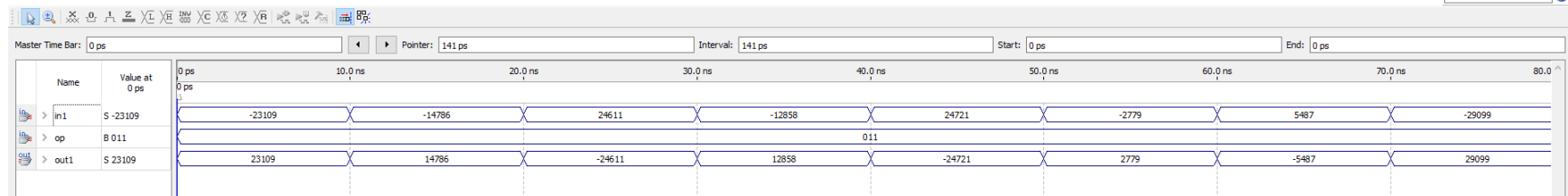

## Multiplexer 2 to 1 (16 bit)

Simulation Waveform Editor - [MyMUX2\_1\_16.sim.vwf (Read-Only)]


File Edit View Simulation Help

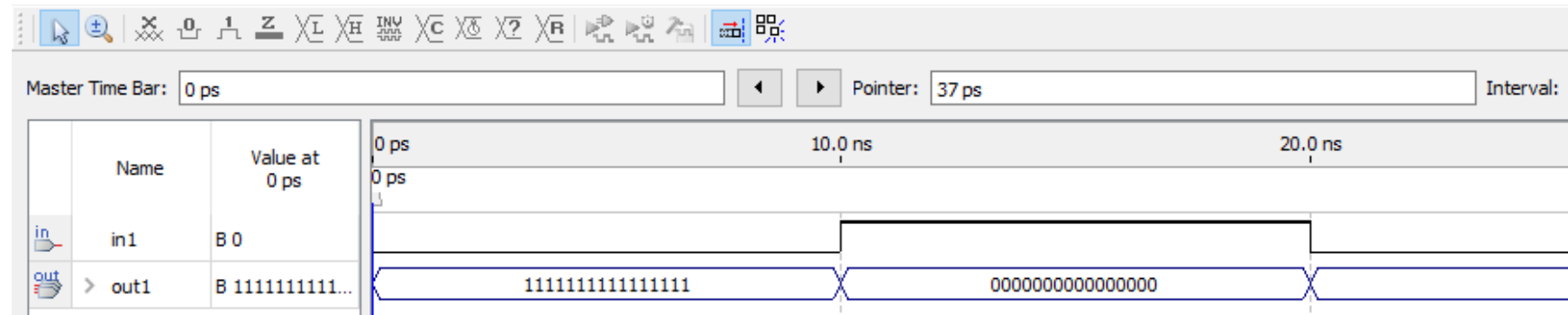

## Full Adder (1 bit) Waveform

Simulation Waveform Editor - [FullAdder.sim.vwf (Read-Only)]


File Edit View Simulation Help

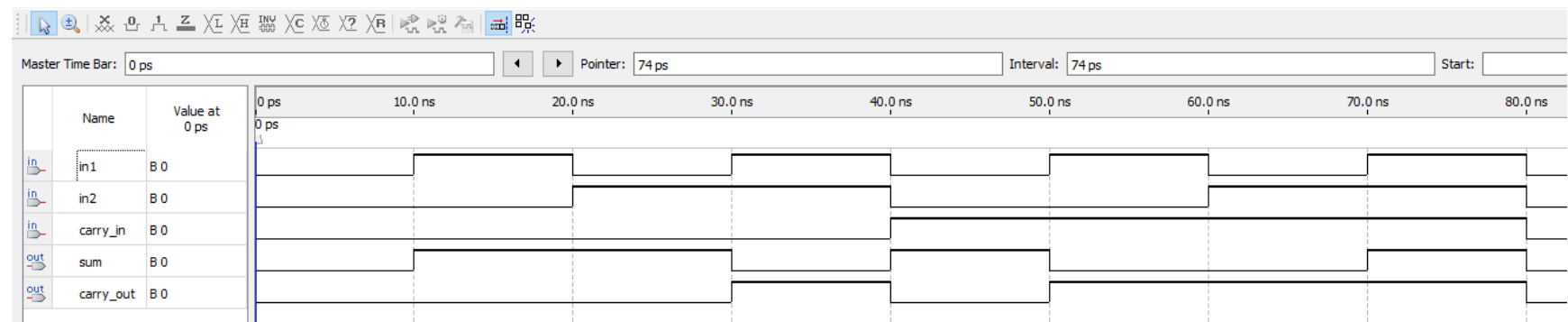


## Full Adder (16 bit) Waveform

Simulation Waveform Editor - [FullAdder16.sim.vwf (Read-Only)]


File Edit View Simulation Help

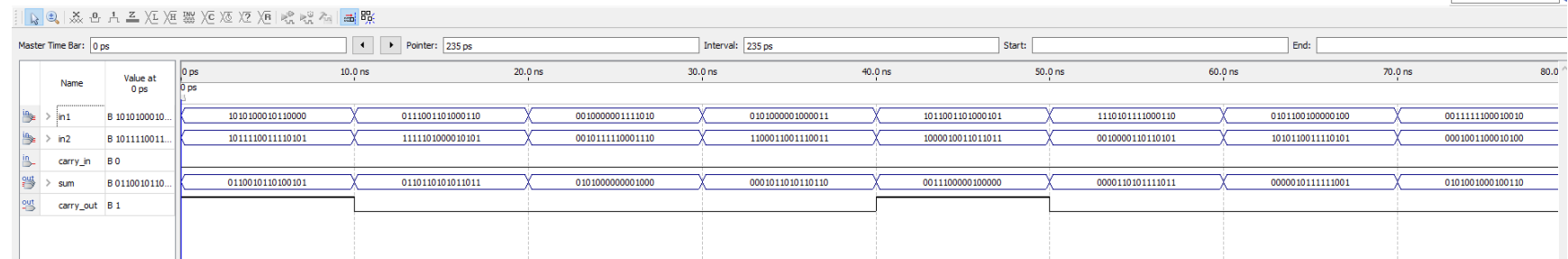


### ALU ADD Waveform

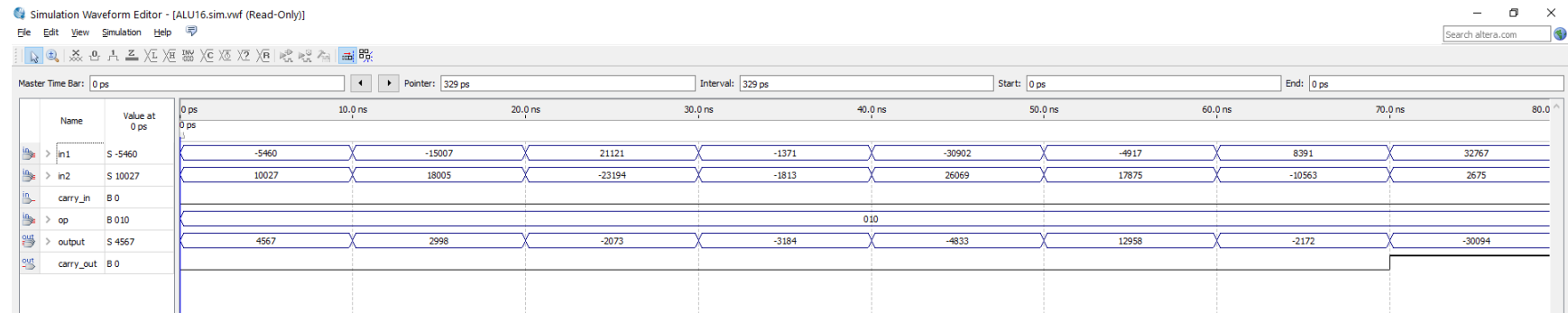


### ALU SUB Waveform

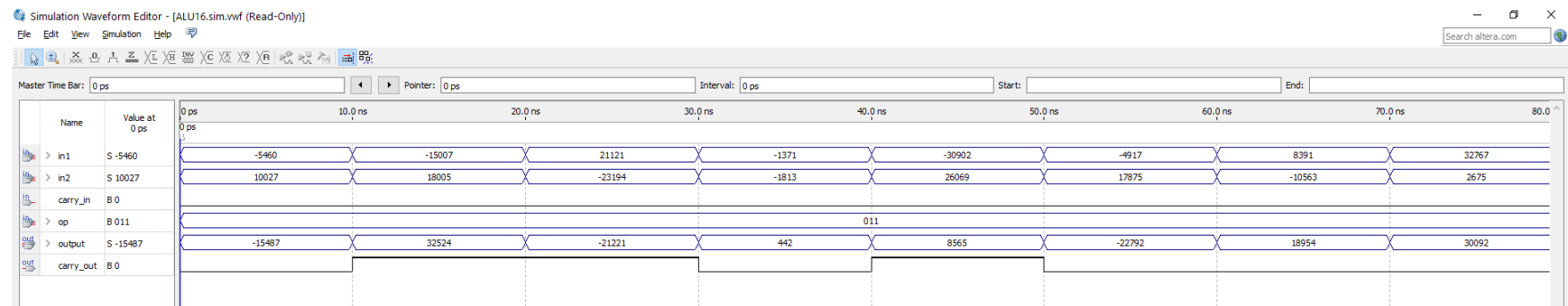


### ALU AND Waveform

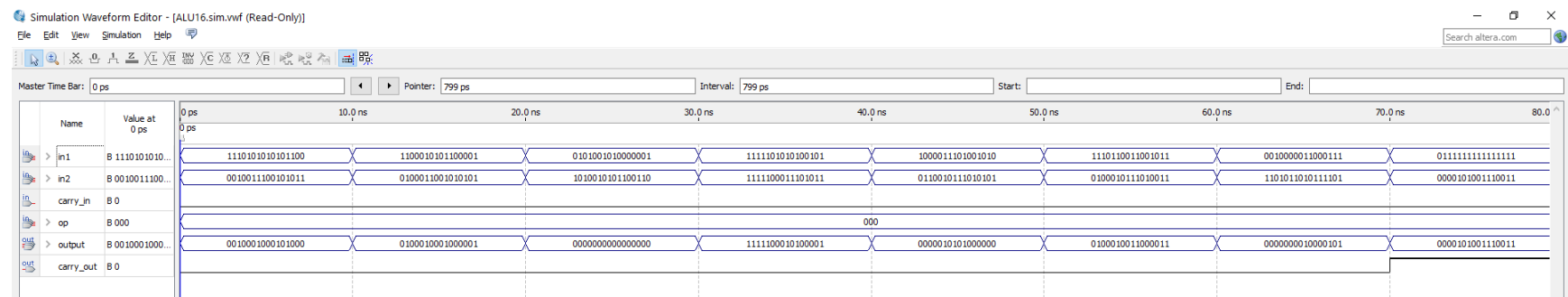

## ALU OR Waveform

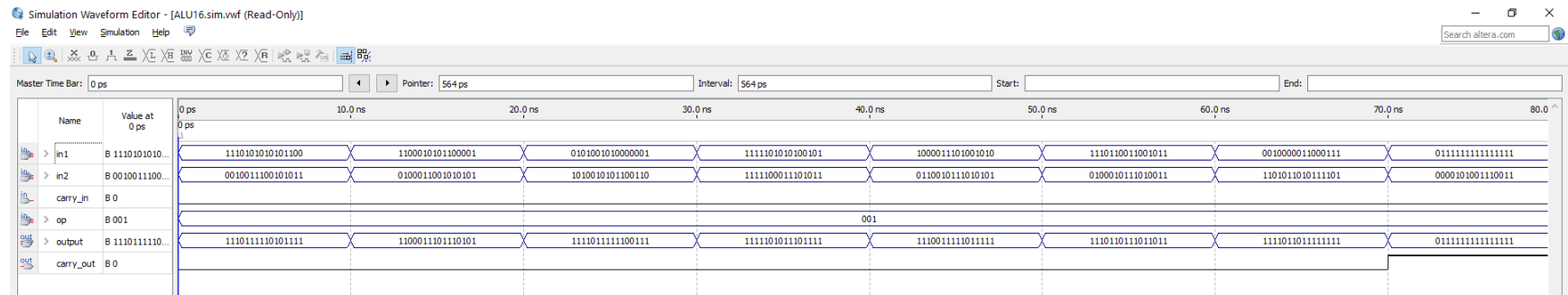

## ALU GEQ Waveform

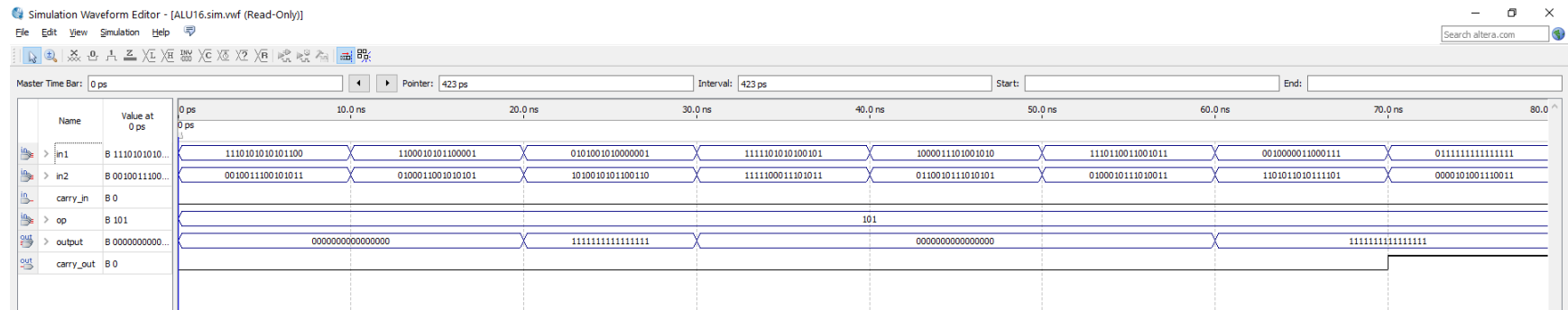

## ALU NOT Waveform

